



INDRAPRASTHA INSTITUTE *of*
INFORMATION TECHNOLOGY
DELHI

Department
of
Electronics & Communication Engineering

ECE111|Digital Circuits
Section: B

Dr S.S. Jamuar

Lab_9:

Shivoy Arora
2021420
28.03.2022

Part A

Aim: To create a UP and DOWN counter with JK Flip Flop

Components/ICs Used: Breadboard, wires, LEDs, resistors, slide switches, power supply, JK Flip Flop, function generator

Link of TINKERCAD Workspace:


UP Counter

<https://www.tinkercad.com/things/lqk4XaMXvWu-tremendous-stantia-migelo/editel?sharecode=66fNR6caJ8rkT-BJaGSME2M6duCZD4cEEfvqjj6pCE>


DOWN Counter

<https://www.tinkercad.com/things/1A2JEMTAeDB-copy-of-part-a-up/editel?sharecode=SPevZjApHsbljdjxhXXKGpvMRvBOesqb3xyZbsgD548w>


Pin Diagram of the IC:

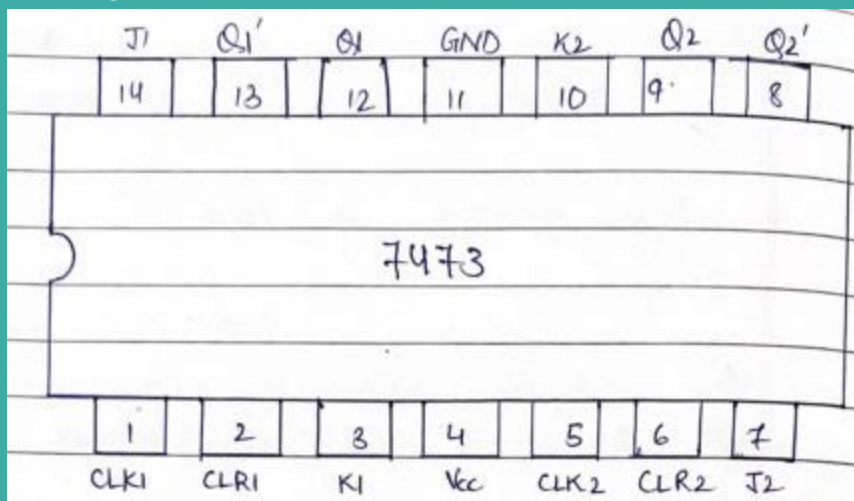

Circuit Diagram: UP Counter

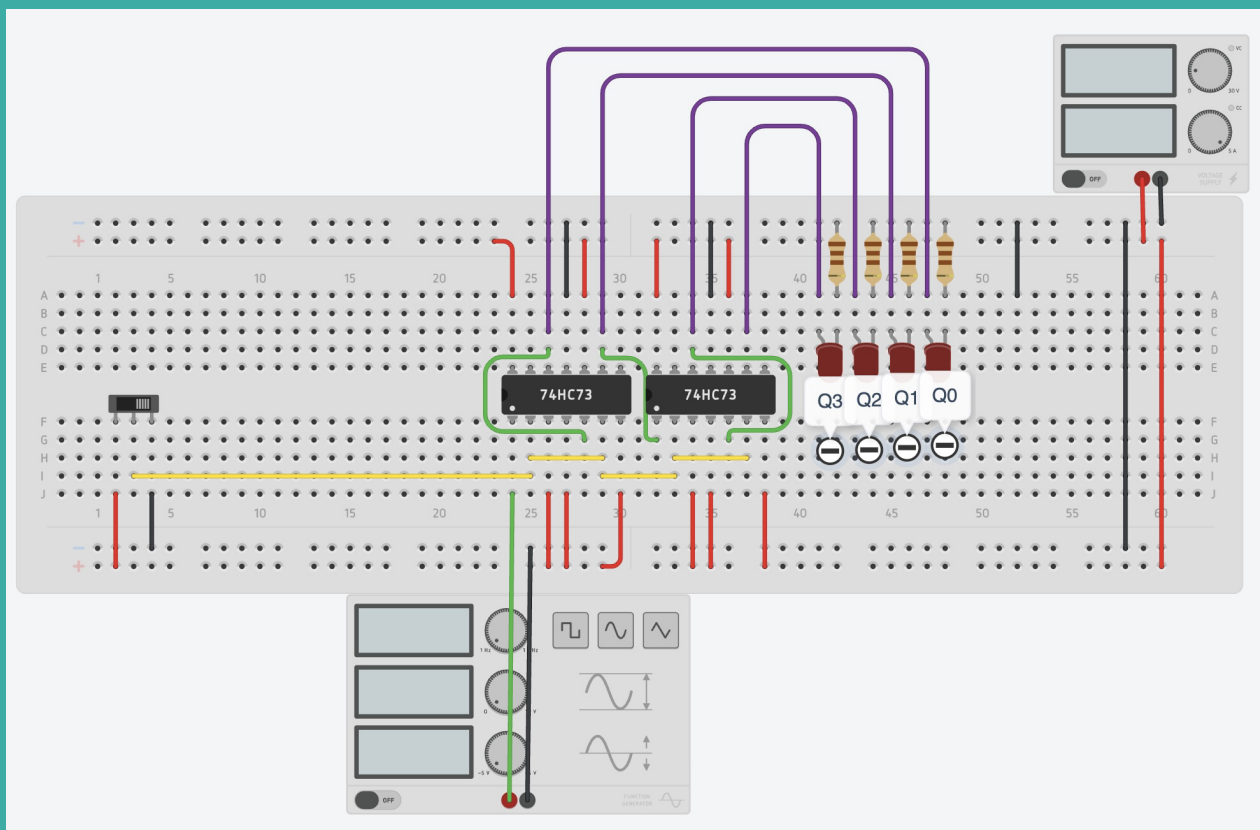

DOWN Counter

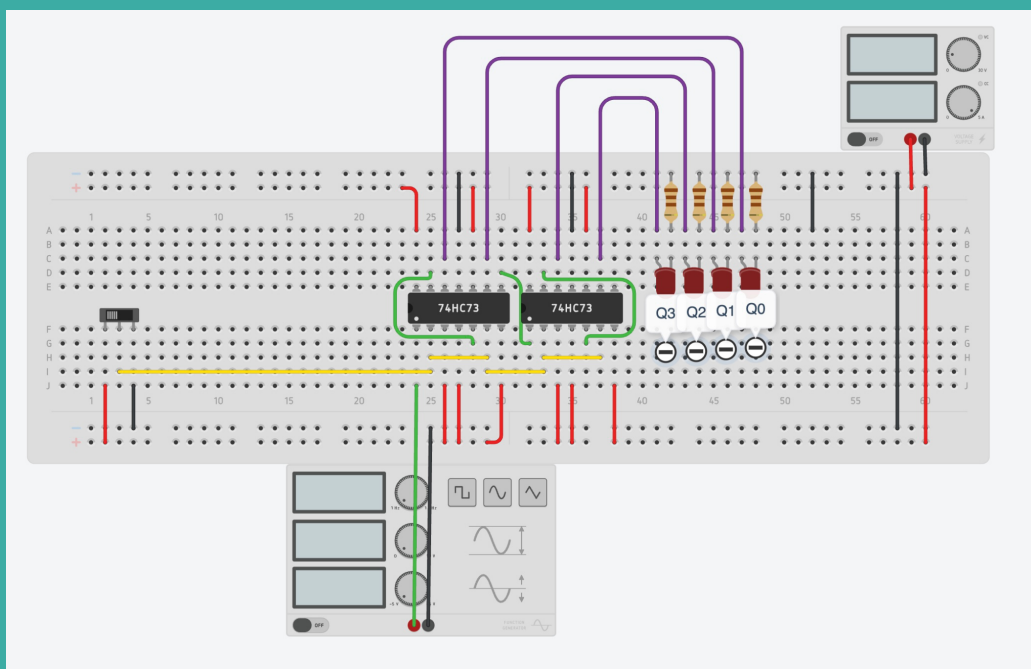

Characteristic equation:

$$Q_n = JQ_{n-1}' + K'Q_{n-1}$$

K maps:

\overline{JK}	0	1
00	1	1
01	1	1
11	1	1
10	1	1

Excitation table:

Q_{n-1}	Q_n	\overline{J}_n	K_n
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0

Observations/Results: A UP and DOWN binary counter is seen

- When $CK1=Q0$, $CK2=Q1$, $CK3=Q2$:
A binary UP counter is observed in which the value of $Q_3Q_2Q_1Q_0$ is observed to be 0000, 0001, 0010, ..., 1111
- When $CK1=Q0'$, $CK2=Q1'$, $CK3=Q2'$:
A binary DOWN counter is observed in which the value of $Q_3Q_2Q_1Q_0$ is observed to be 1111, 1110, 1101, ..., 0000

Application:

- It is used to count the number of pulses inputted in the first clock by the function generator
- They can also be used as a binary clock

Part B


Aim: To create a decade ripple counter

Components/ICs Used: Breadboard, wires, LEDs, resistors, slide switches, power supply, function generator, JK Flip Flop, NAND gate, 7 segment decoder, 7 segment display


Link of TINKERCAD Workspace:

<https://www.tinkercad.com/things/kx1BoP9xE05-copy-of-lab09-partb/editel?sharecode=b5l3nGmChL4u8blvxBmrawepHyXRkH-7RMKEqZDrqTc>

Pin Diagram of the IC:

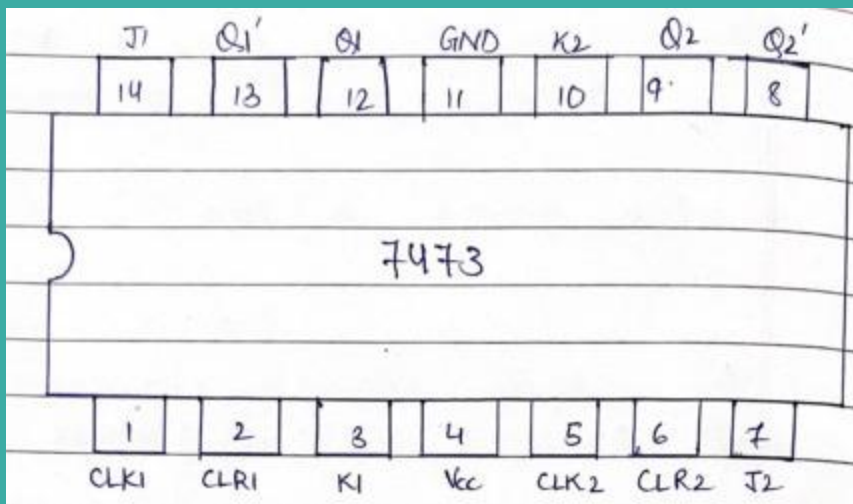

Circuit Diagram:

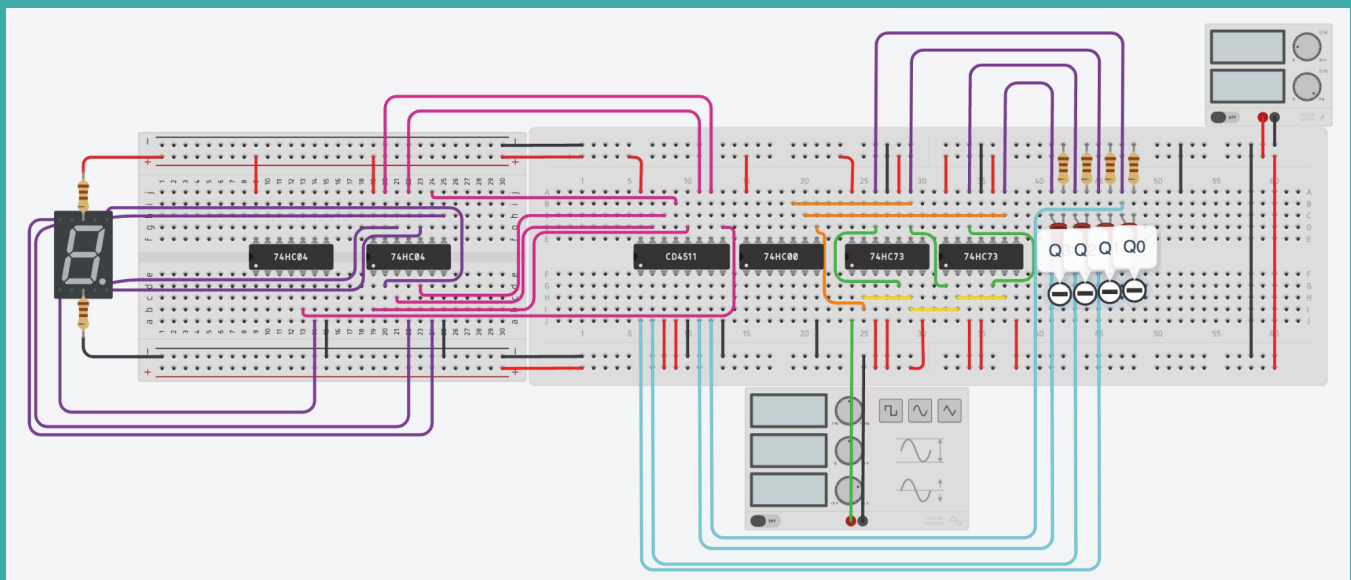

Characteristic equation:

$$Q_n = JQ_{n-1}' + K'Q_{n-1}$$

K maps:

JK \ Q_0	0	1
00	0	1
01	0	0
11	1	0
10	1	0

Excitation table:

Q_{n-1}	Q_n	J_n	K_n
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0

Observations/Results:

A binary UP counter is observed in which the value of $Q_3Q_2Q_1Q_0$ is observed to be 0000, 0001, 0010, ..., 1001 which is then decoded to decimal form and is shown via a 7 segment display

Application:

- It is used to count the number of pulses inputted in the first clock by the function generator
- They can also be used as a binary clock