



INDRAPRASTHA INSTITUTE *of*
INFORMATION TECHNOLOGY
DELHI

Department
of
Electronics & Communication Engineering

ECE111|Digital Circuits
Section: B

Dr S.S. Jamuar

Lab_6:

Shivoy Arora
2021420
2.03.22

Part A


Aim: To decrypt a communication encryption and see it in seven segment display


Components/ICs Used: 4x1 MUX, 7 segment display, NAND, NOR, AND, OR, 3-input AND, 4-input OR, 5-input OR gates

Link of CIRCUITVERSE Workspace:



<https://circuitverse.org/simulator/edit/lab06-9d92dd0b-18f1-4079-af76-5af4b7029aba>



Pin Diagram of the IC:

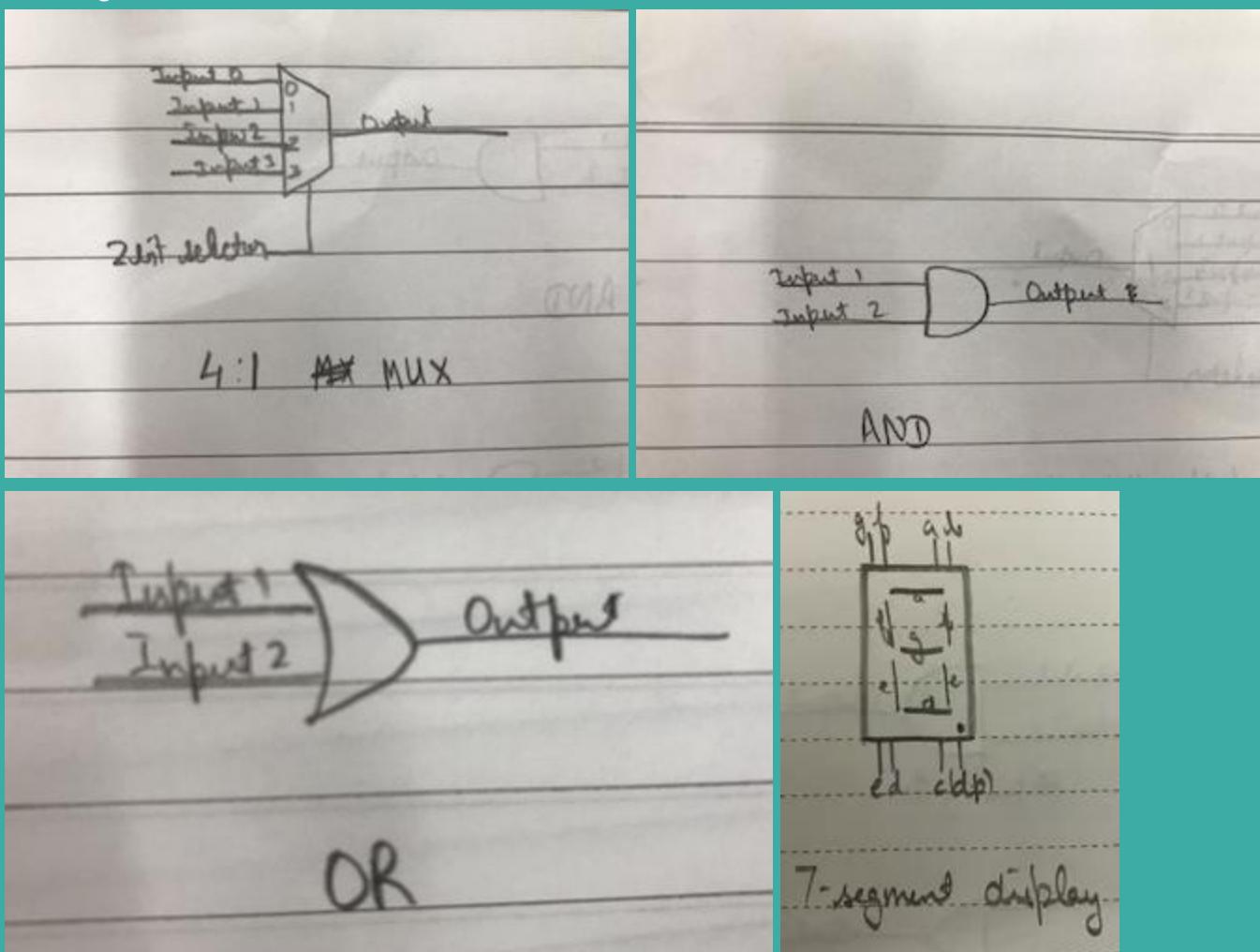

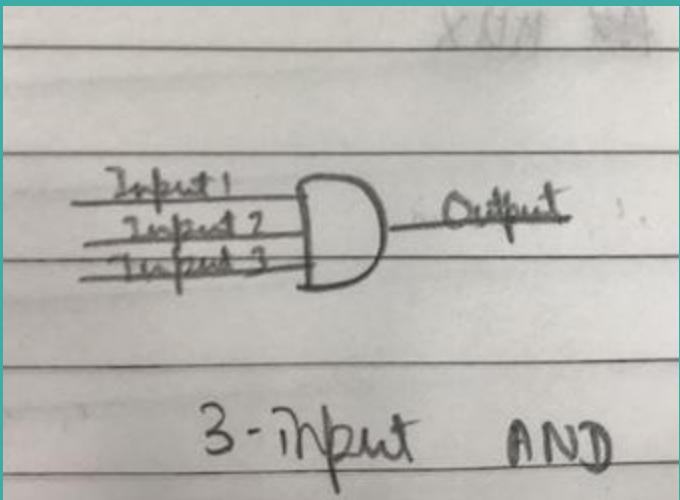


3 - Input AND

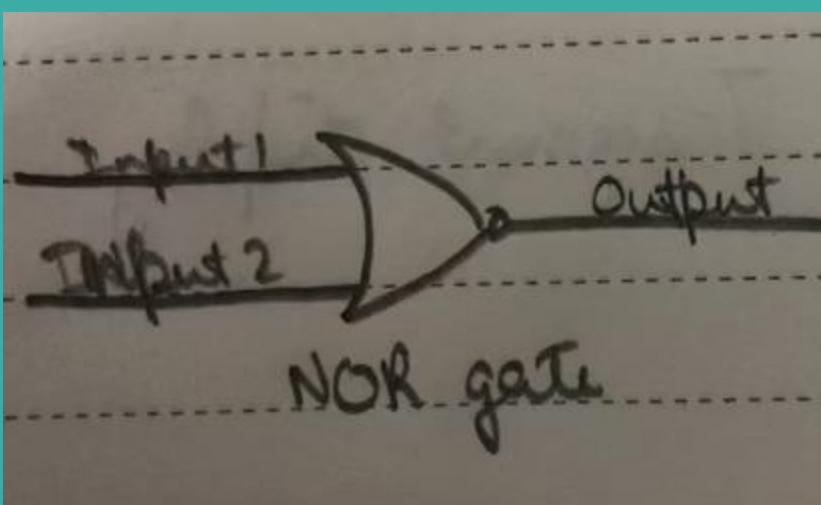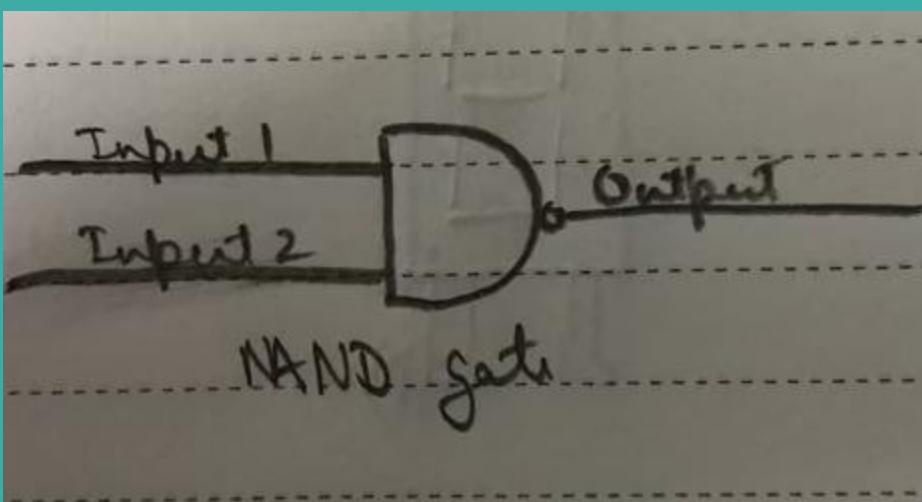

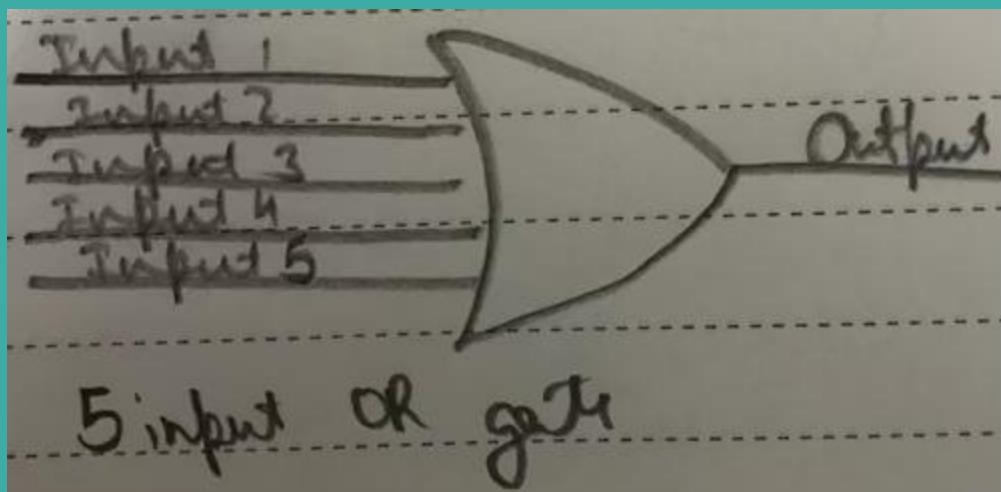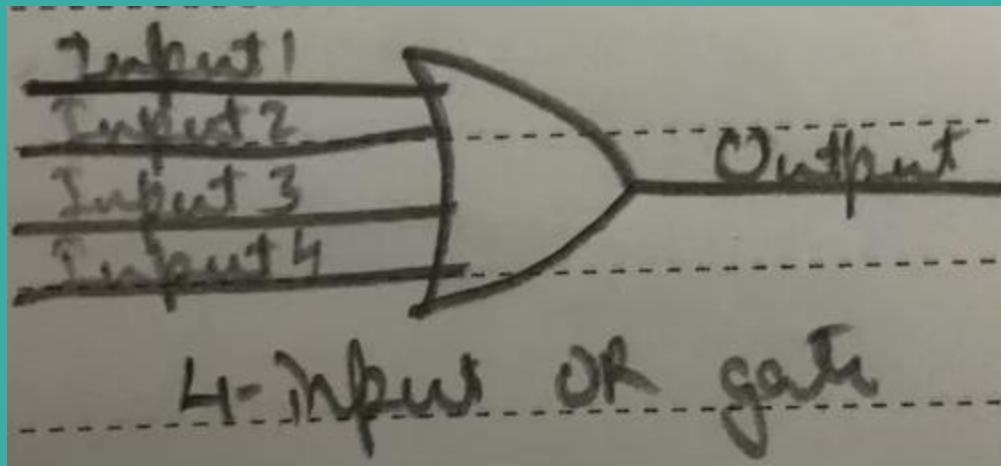

Circuit Diagram:

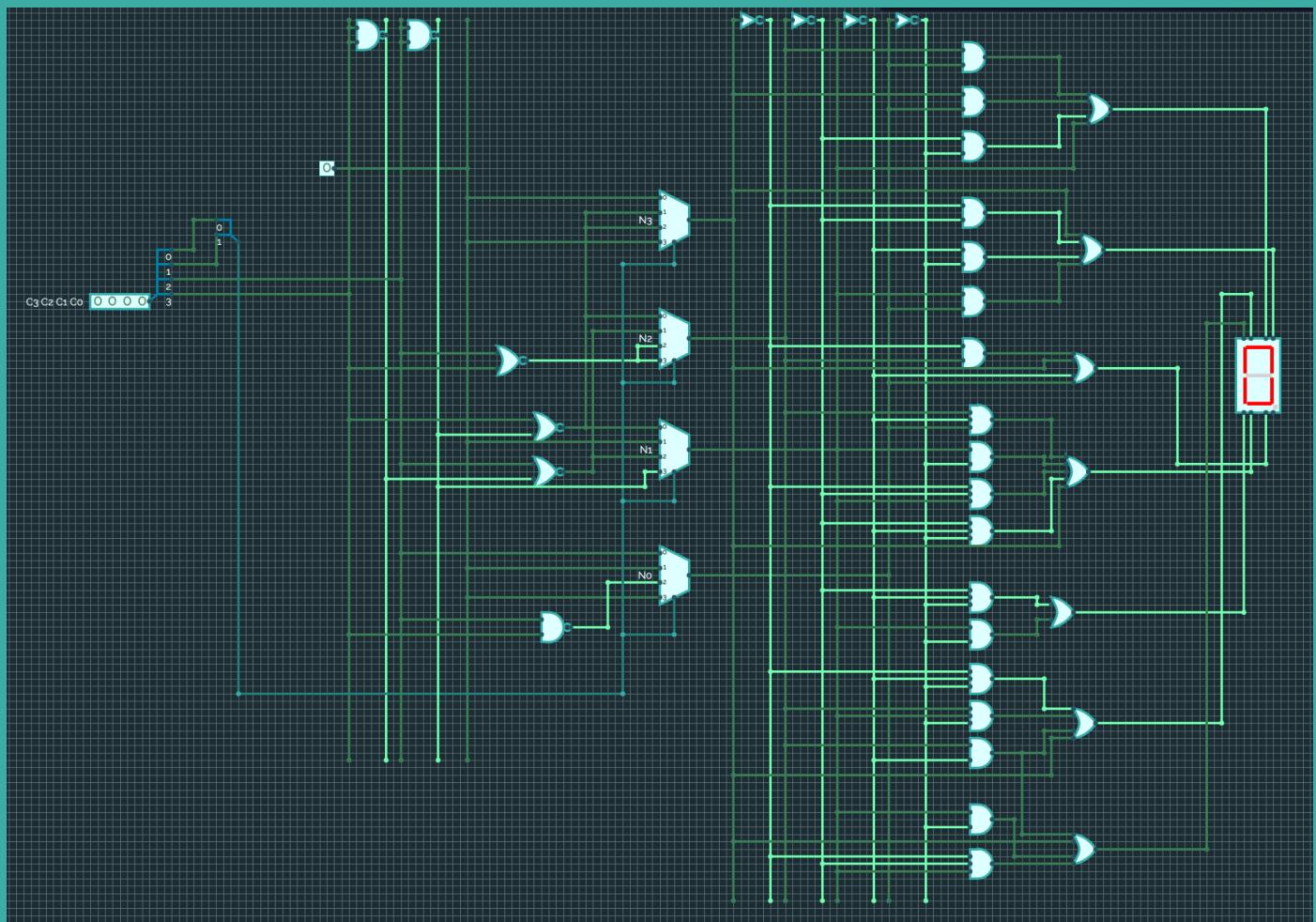


K maps and Truth Table:

$$(C_3 C_2 C_1 C_0)_2 = (13 - N)_{10} \quad \# 4 > N \geq 0$$


$$(C_3 C_2 C_1 C_0)_2 = (N - 3)_{10} \quad \# 9 > N \geq 5$$




C_1	C_0	No
0	0	C_2
0	1	0
1	0	$\bar{C}_3 + \bar{C}_2$
1	1	0

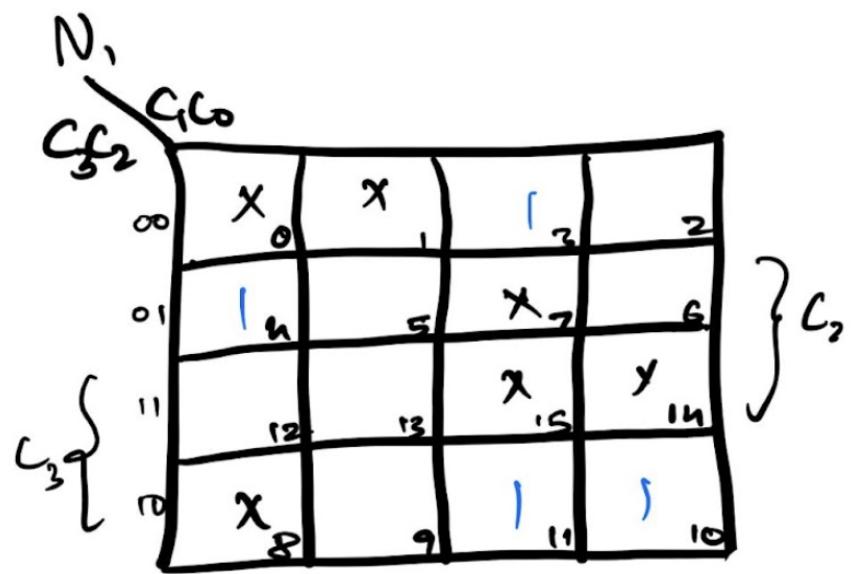


C_1	C_0	N_1
0	0	$\bar{C}_3 C_2$
0	1	0
1	0	$C_3 \bar{C}_2$
1	1	\bar{C}_2

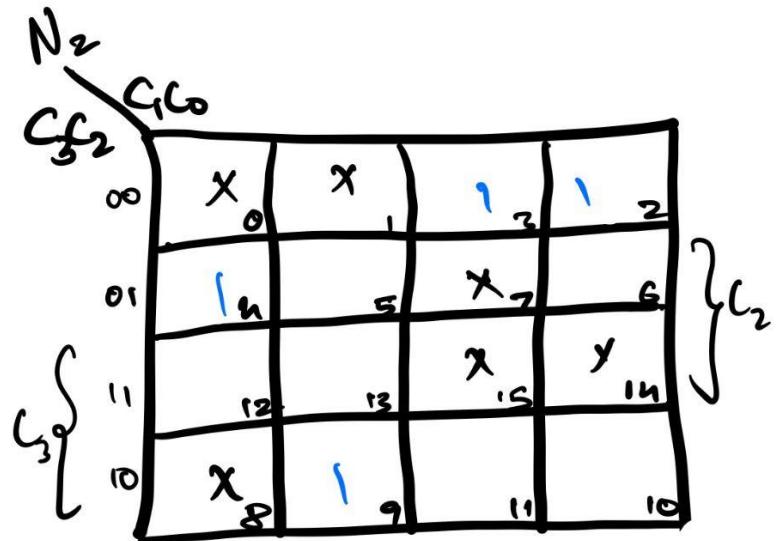


C_1	C_0	N_2
0	0	$\bar{C}_3 \bar{C}_2$
0	1	$C_3 \bar{C}_2$
1	0	$\bar{C}_3 \bar{C}_2$
1	1	$\bar{C}_3 \bar{C}_2$

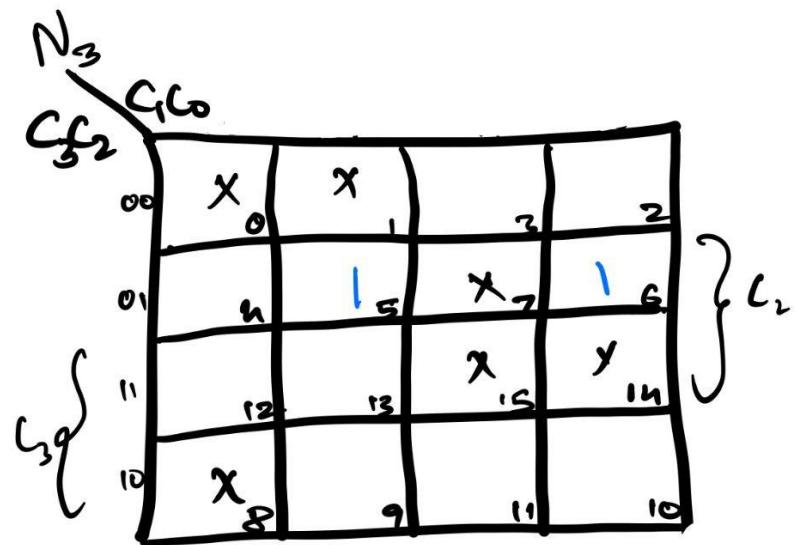



C_1	C_0	N_3
0	0	0
0	1	$\bar{L}_3 L_2$
1	0	$\bar{L}_3 L_2$
1	1	0

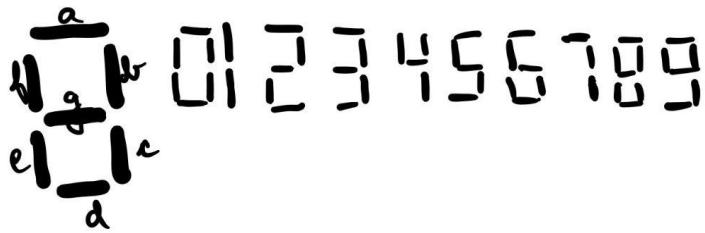


N_3	N_2	N_1	N_0	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1

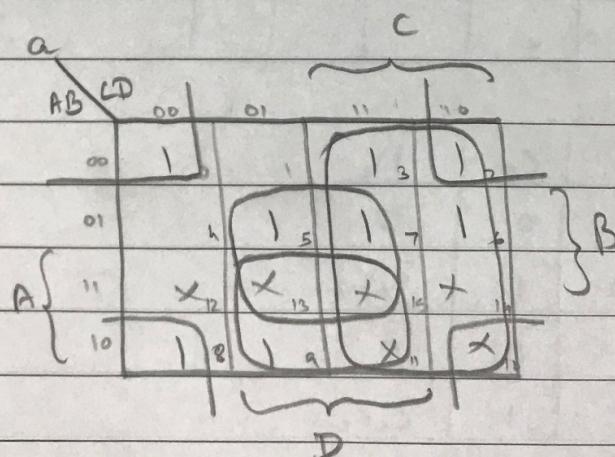

$$a = BD + AD + \bar{B}\bar{D} + C$$

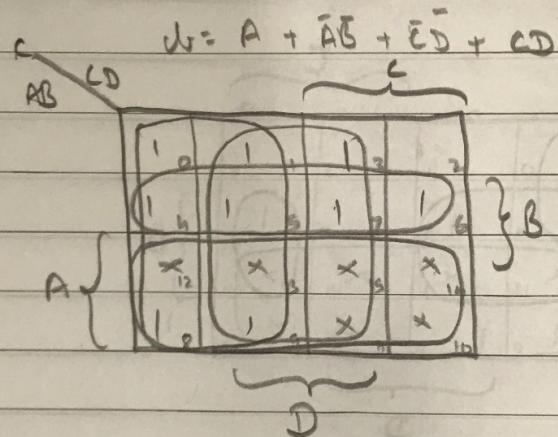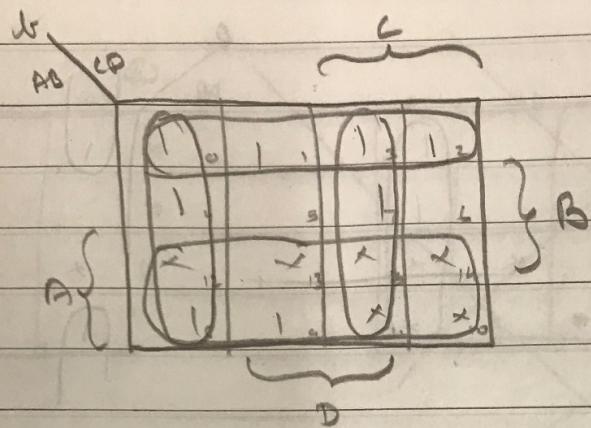

$$c = A + D + \bar{C} + \bar{A}B$$

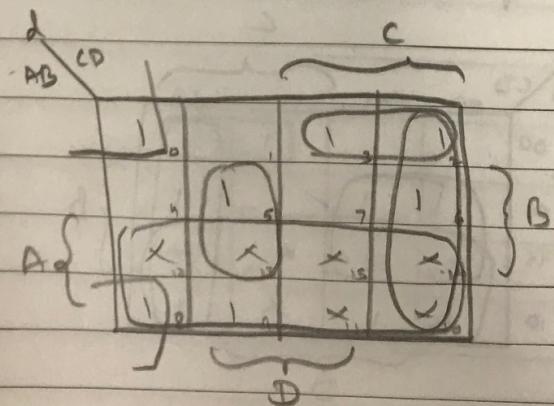

$$d = A + B\bar{C}D + C\bar{D} + \bar{A}\bar{B}C + \bar{A}\bar{C}\bar{D}$$

e
AB CD

00 01 11 10

00 01 11 10

11 10 11 10

11 10 11 10

11 10 11 10

11 10 11 10

11 10 11 10

11 10 11 10

11 10 11 10

11 10 11 10

11 10 11 10

11 10 11 10

11 10 11 10

11 10 11 10

11 10 11 10

e
AB CD

00 01 11 10

00 01 11 10

11 10 11 10

11 10 11 10

11 10 11 10

11 10 11 10

11 10 11 10

11 10 11 10

11 10 11 10

11 10 11 10

11 10 11 10

11 10 11 10

11 10 11 10

11 10 11 10

11 10 11 10

$$e = A + \bar{C}\bar{D} + \bar{B}\bar{C}\bar{D}$$

$$e = \bar{B}\bar{C}\bar{D} + C\bar{D}$$

f
AB CD

00 01 11 10

00 01 11 10

11 10 11 10

11 10 11 10

11 10 11 10

11 10 11 10

11 10 11 10

11 10 11 10

11 10 11 10

11 10 11 10

11 10 11 10

E

B

D

$$f = A + B\bar{C} + \bar{A}\bar{C}\bar{D} + BC\bar{D}$$

g
AB CD

00 01 11 10

00 01 11 10

11 10 11 10

11 10 11 10

11 10 11 10

11 10 11 10

C

B

D

$$g = A + B\bar{C} + \bar{A}\bar{B}C + C\bar{D}$$

Part B







Aim: To create a circuit to divide two numbers and get the quotient and remainder

Components/ICs Used: Input, Output, AND, OR, NOT, Gate, splitter, 4:1 MUX


Link of Circuitverse Workspace:

<https://circuitverse.org/simulator/edit/lab06-9d92dd0b-18f1-4079-af76-5af4b7029aba>

Pin Diagram of the IC:

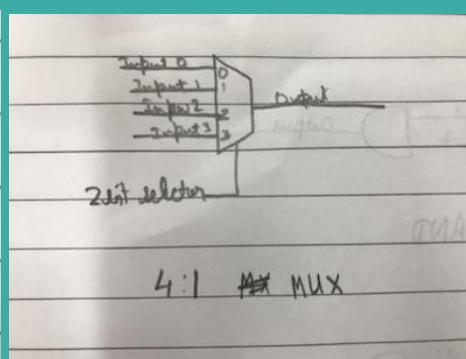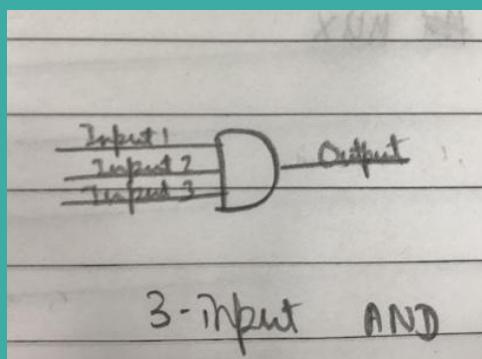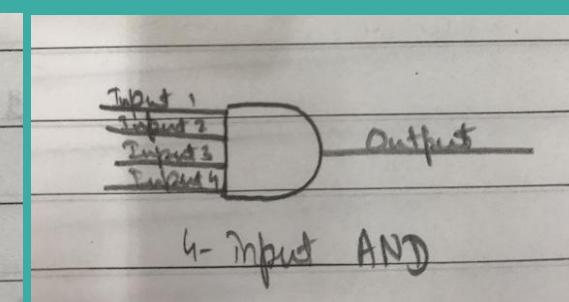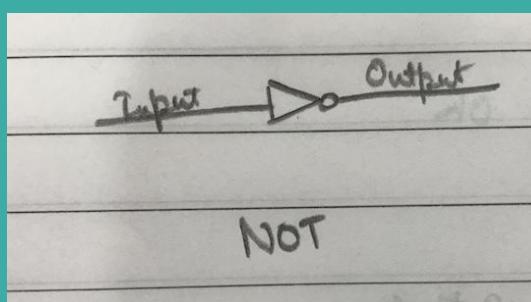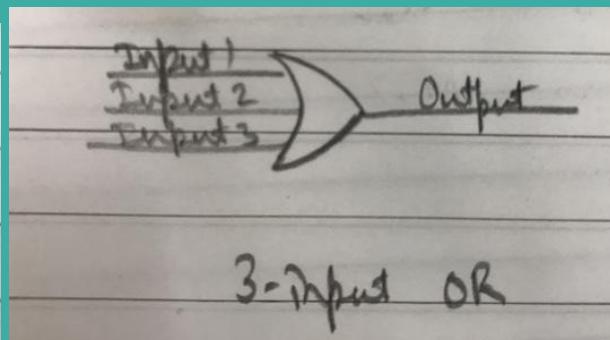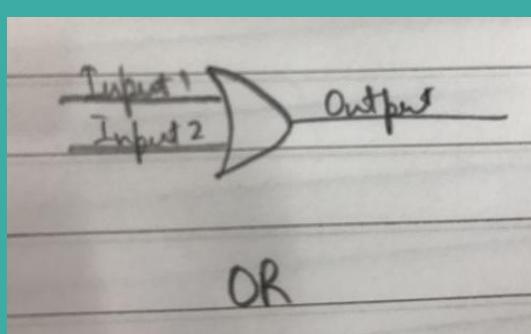



Circuit Diagram:

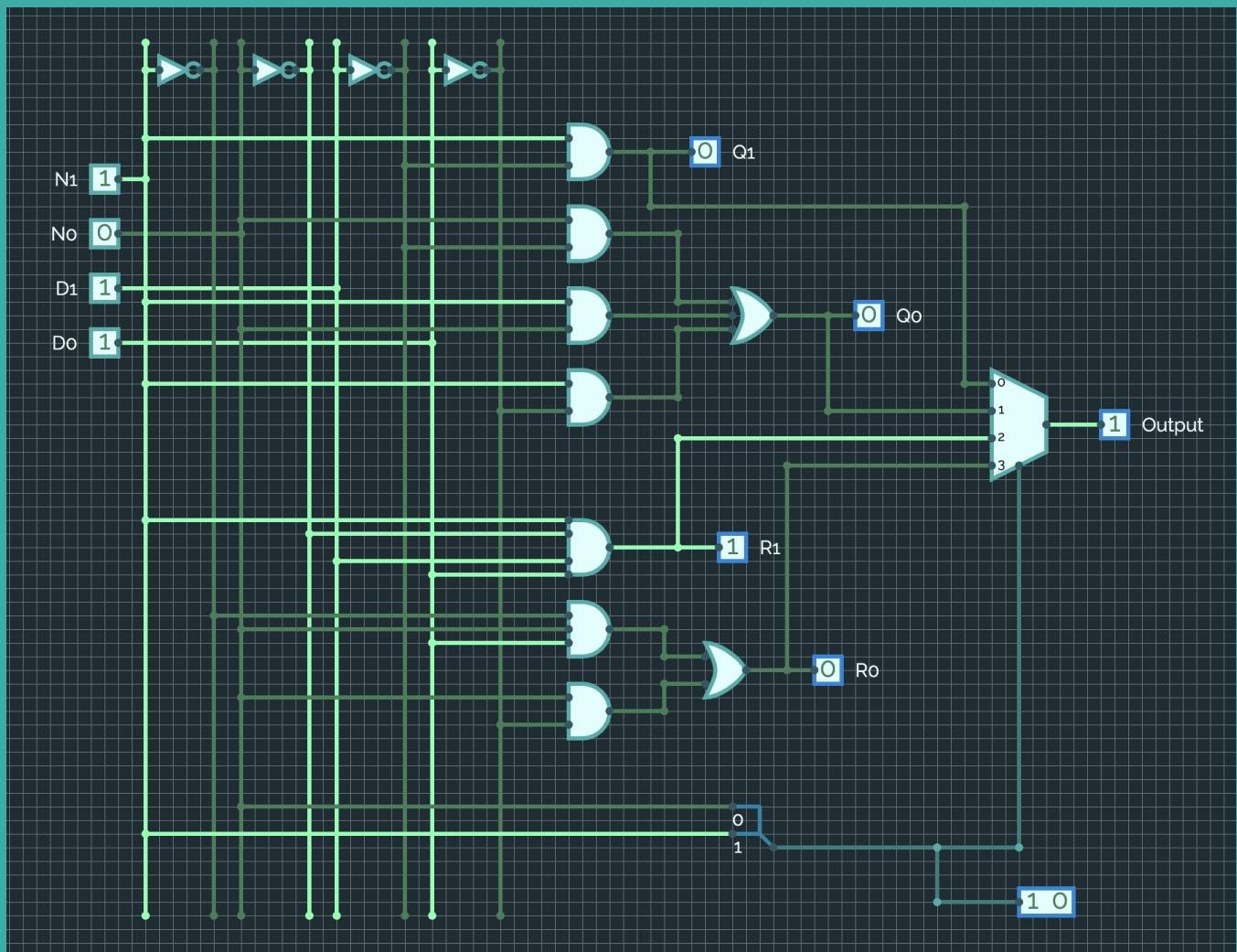

Truth Table:

4-Bit									
N1	N0	D1	D0	Q1	Q0	R1	R0		
0	0	0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	0	0	0
0	0	1	0	0	0	0	0	0	0
0	0	1	1	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0
0	1	0	1	0	0	1	0	0	0
0	1	1	0	0	0	0	0	0	1
0	1	1	1	0	0	0	0	0	1
1	0	0	0	0	0	0	0	0	0
1	0	0	1	1	0	0	0	0	0
1	0	1	0	0	0	1	0	0	0
1	0	1	1	1	0	0	1	0	0
1	1	0	0	0	0	0	0	0	0
1	1	0	1	1	1	1	0	0	0
1	1	1	0	0	0	1	0	0	1
1	1	1	1	1	0	1	1	0	0
1	1	1	1	1	0	1	0	0	0

K maps:

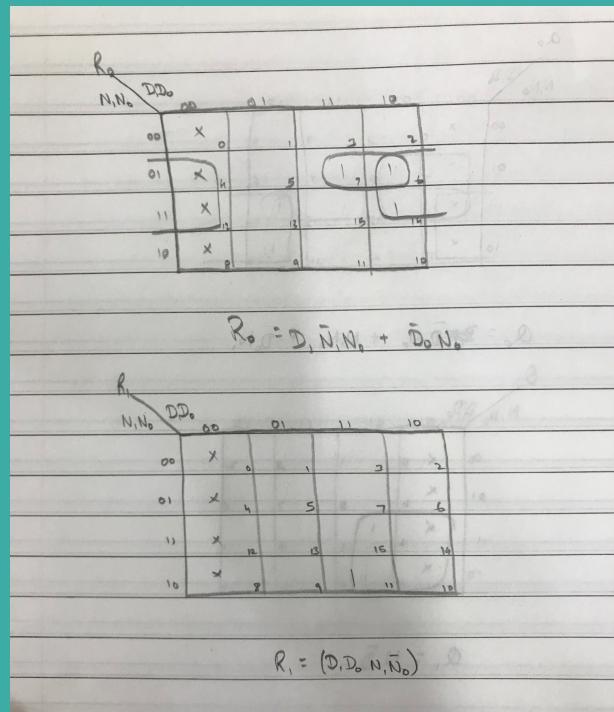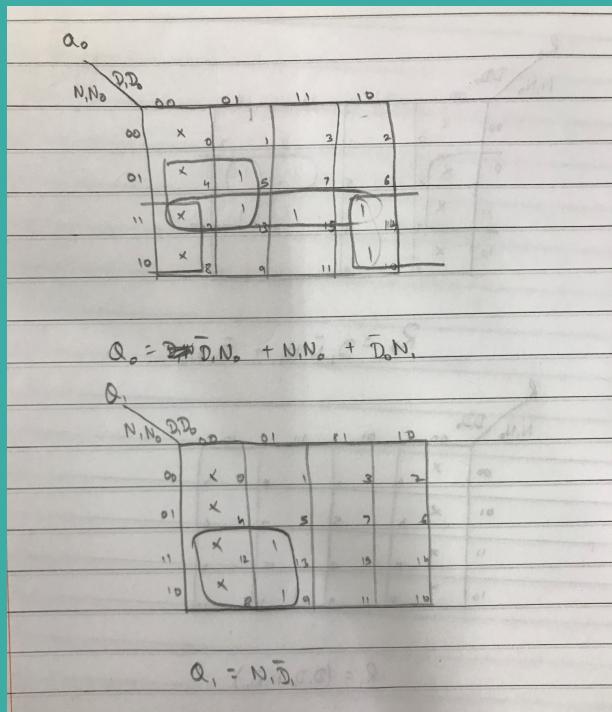

Observations/Results: Got the quotient and remainder after dividing two 2-bit binary numbers

Application: Dividing two 2-bit binary numbers