



INDRAPRASTHA INSTITUTE *of*
INFORMATION TECHNOLOGY
DELHI

Department
of
Electronics & Communication Engineering

ECE111|Digital Circuits
Section: B

Dr S.S. Jamuar

Lab_8:

Shivoy Arora
2021420
21.03.22

Part A


Aim: To create a JK flip flop and find the output for the given sequence

Components/ICs Used: Breadboard, wires, LEDs, resistors, slide switches, power supply, JK Flip Flop, function generator


Link of TINKERCAD Workspace:

<https://www.tinkercad.com/things/0UctMx8bk8X-stunning-habbi-jaban/editel?sharecode=iUqnAIXEEhRW4ou0dHtdSSbQ66fy9Ia2eeKoolR4R0Y>

Pin Diagram of the IC:

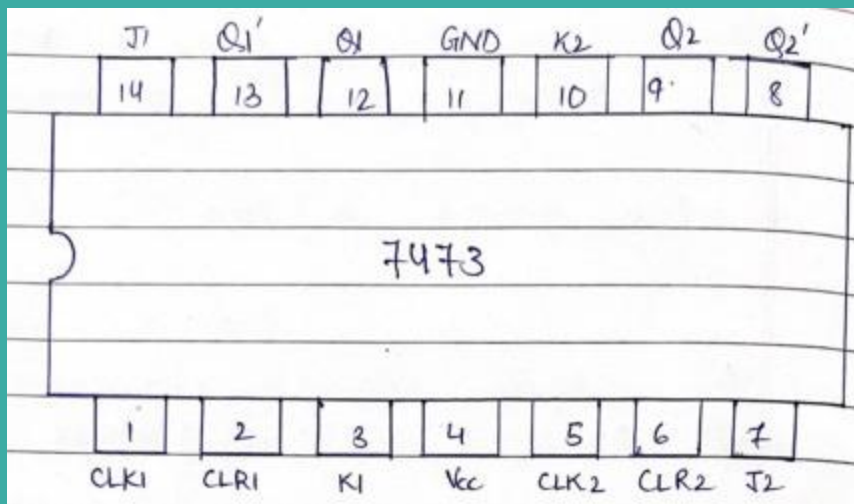

Circuit Diagram:

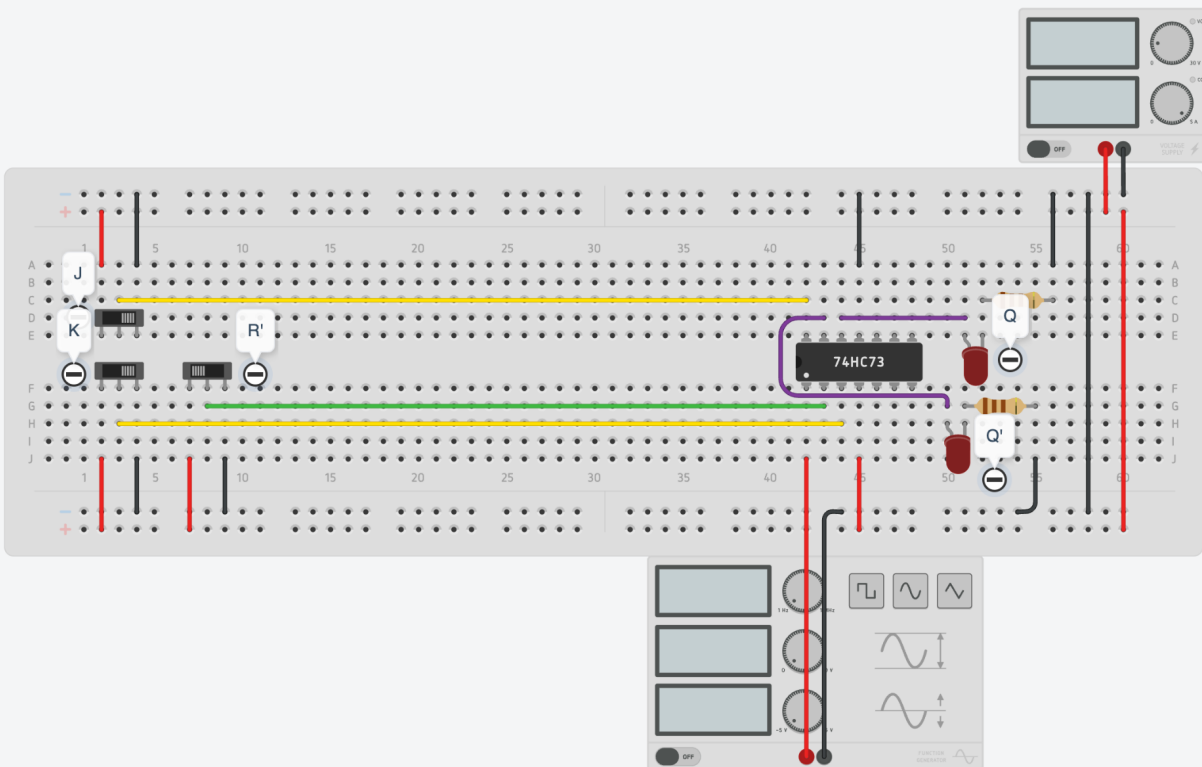

Truth Table:

J	K	Q	Q'
0	1	0	1
0	0	0	1
1	0	1	0
0	0	1	0
0	1	0	1
1	1	1	0
1	0	1	0
1	1	0	1
0	1	0	1

Characteristic equation:

$$Q_n = JQ_{n-1}' + K'Q_{n-1}$$

K maps:

JK \ Q	0	1
00		1
01		1
11	1	
10	1	1

Excitation Table:

Q_{n-1}	Q_n	J_n	K_n
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0

Observations/Results: The working of JK flip flop is seen and the output for the given sequence is obtained

Application:

- JK flip flop is used to store a bit of data
- JK flip flop fixes the invalid state of SR flip flop

Part B


Aim: To check the outputs of D flip flop

Components/ICs Used: Breadboard, wires, LEDs, resistors, slide switches, power supply, D flip flop, function generator


Link of TINKERCAD Workspace:

<https://www.tinkercad.com/things/d4VacHJP32q-exquisite-fyyran/editel?sharecode=FEU0mPDTKKIe48yLwtPq5QNden13q9HwummrRB9Lk-Q>

Pin Diagram of the IC:

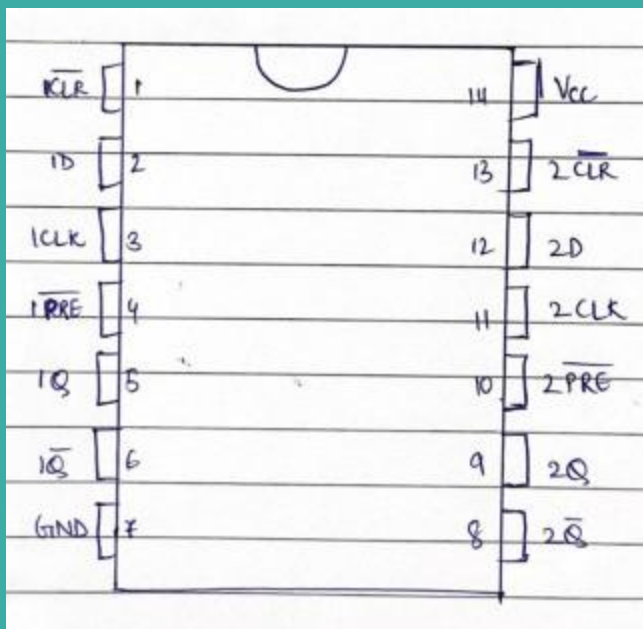

Circuit Diagram:

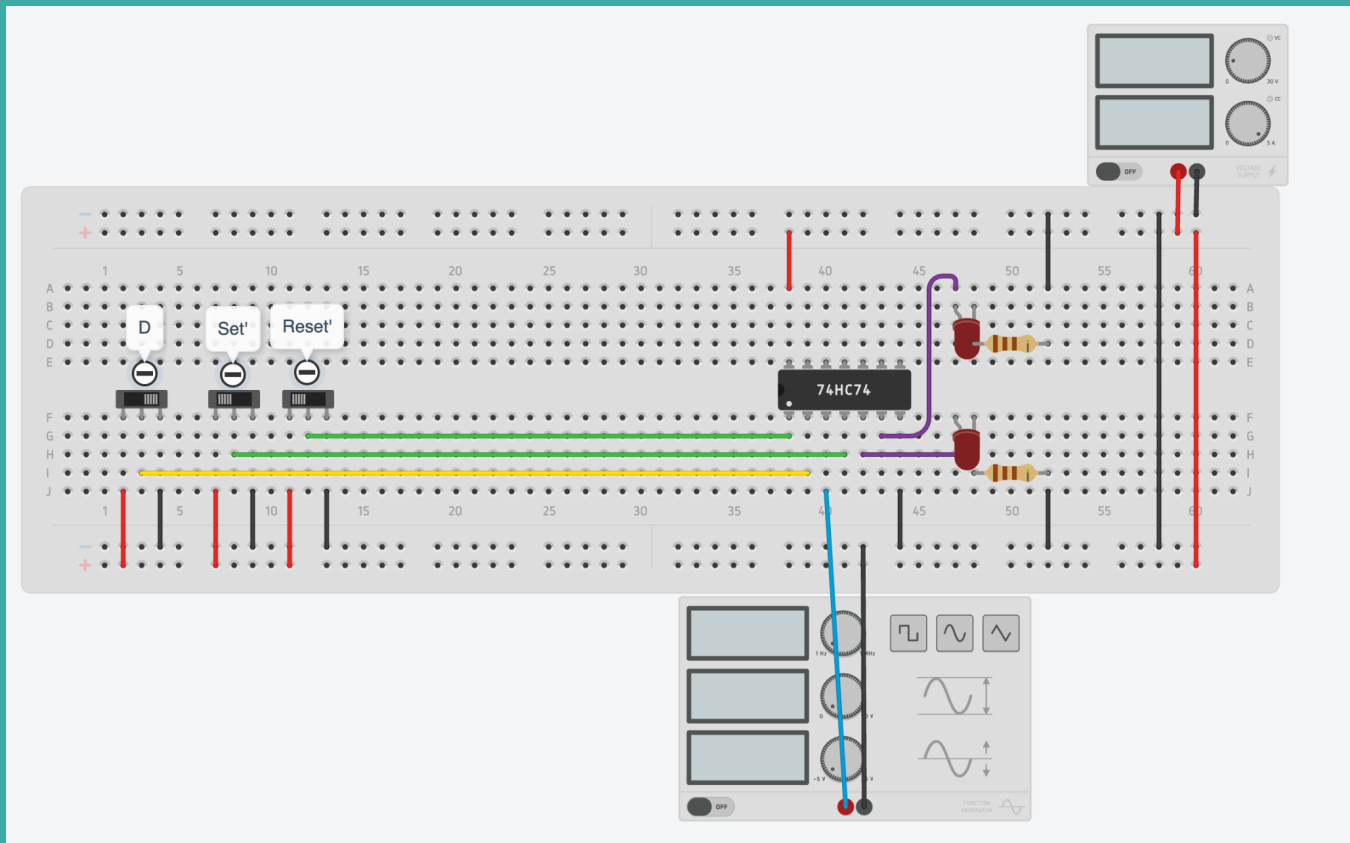


Truth Table:

Set'	Reset'	D	clk	Q	Q'
0	1	∅	∅	1	0
1	0	∅	∅	0	1
0	0	∅	∅	1	1
1	1	1	↑	1	0
1	1	0	↑	0	1

Characteristic equation:

$$Q_n = D$$

K maps:

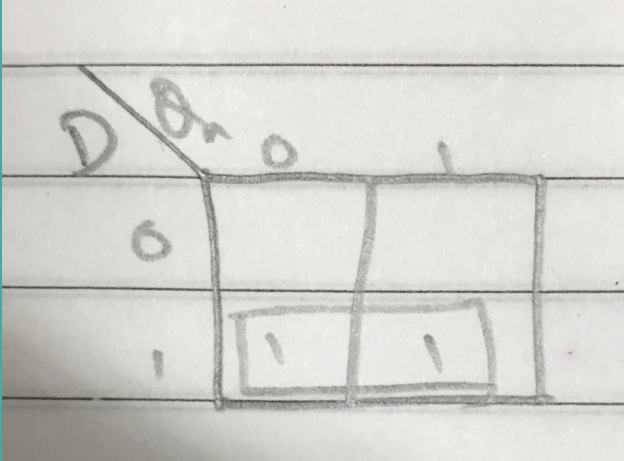

D \ Q _n	0	1
0		
1	1	1

Observations/Results: The working of D flip flop is seen

Application:

- D flip-flop can be used to create delay-lines which are used in digital signal processing systems.
- D flip-flops used as data synchronizers