



INDRAPRASTHA INSTITUTE *of*
INFORMATION TECHNOLOGY
DELHI

Department
of
Electronics & Communication Engineering

ECE111|Digital Circuits
Section: B

Dr S.S. Jamuar

Lab_2:

Shivoy Arora
2021420
24 Jan 2022

Part A: DeMorgan's theorem

Aim: To verify DeMorgan's law



Components/ICs Used: Breadboard, led, wires, slide switch, led, resistors, NOR Gate, AND, gate, NAND gate, OR gate, power supply.

Link of TINKERCAD Workspace (if applicable):

[\$Y=\(A+B\)'\$](#)


[\$Y=\(A.B\)'\$](#)

Pin Diagram of the IC (If Applicable):

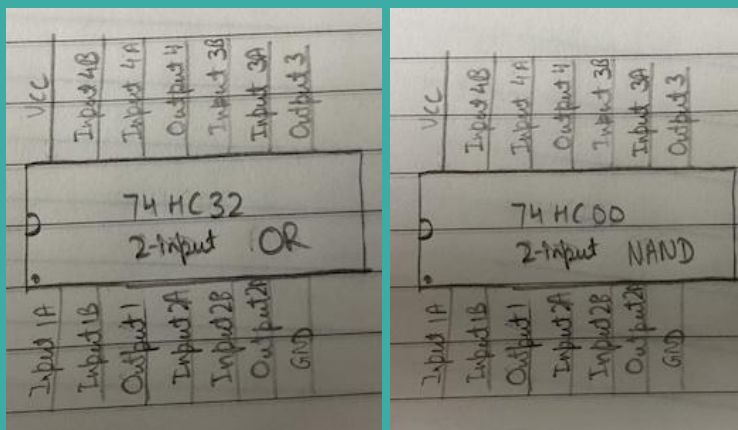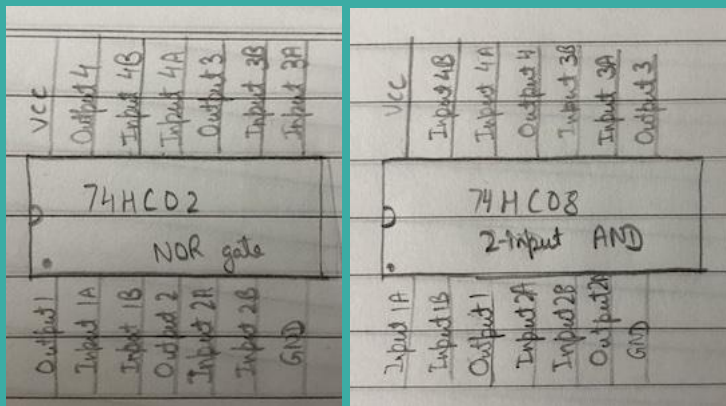


Circuit Diagram: (Screenshot of Circuitverse/TinkerCAD workspace)

$$Y = (A+B)' = A'B'$$

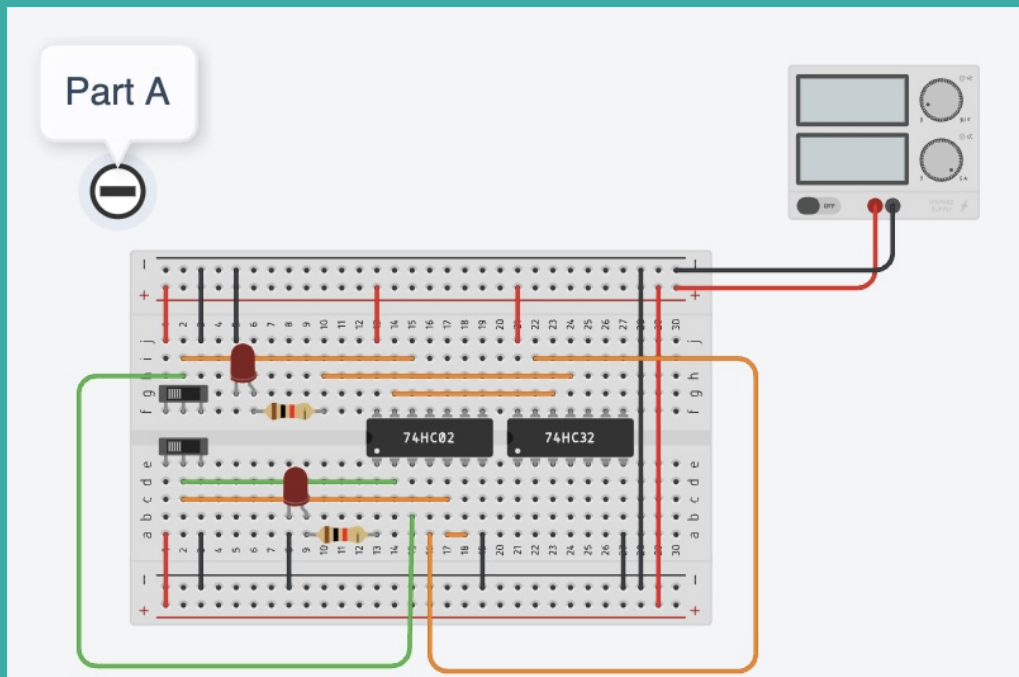

$$Y = (A.B)' = A'+B'$$

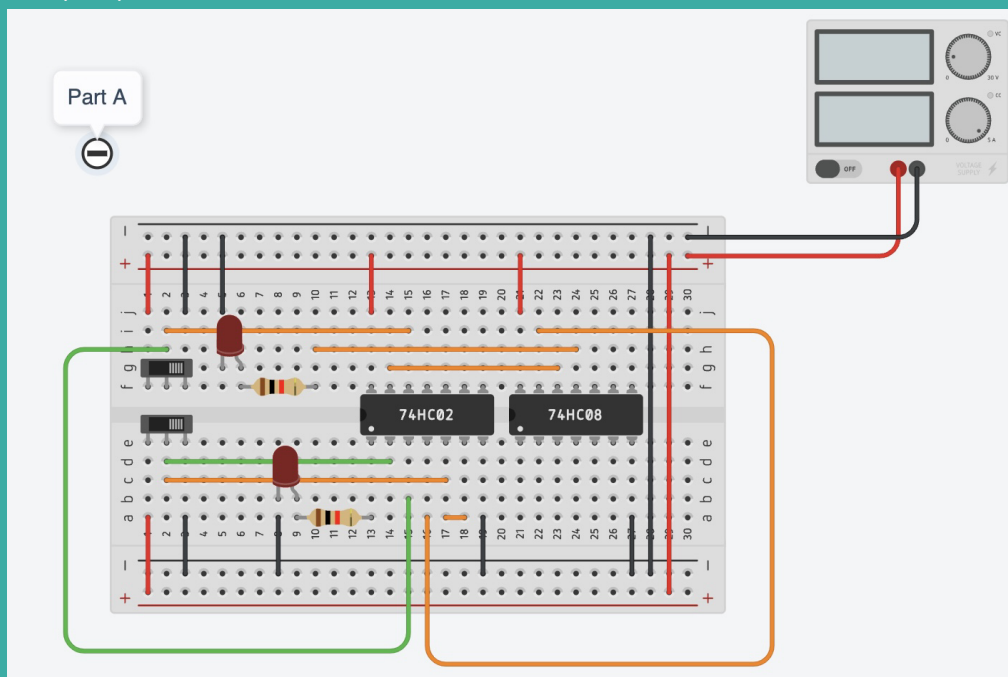

Truth Table:

$$Y = (A+B)' = A'*B'$$

A	B	A'	B'	(A+B)'	A'*B'
0	0	1	1	1	1
0	1	1	0	0	0
1	0	0	1	0	0
1	1	0	0	0	0

$$Y = (A*B)' = A' + B'$$

A	B	A'	B'	(A*B)'	A'+B'
0	0	1	1	1	1
0	1	1	0	1	1
1	0	0	1	1	1
1	1	0	0	0	0

Observations/Results: DeMorgan's law is verified

Application: DeMorgan's law is used to simplify circuits


Part B: Binary Half Alder

Aim: To create binary half alder circuit in tinkercad


Components/ICs Used: Breadboard, wires, power supply, resistors, LEDs, slide switches, AND gate, XOR gate.

Link of TINKERCAD Workspace (if applicable): [Half-Alder](#)

Pin Diagram of the IC (If Applicable):

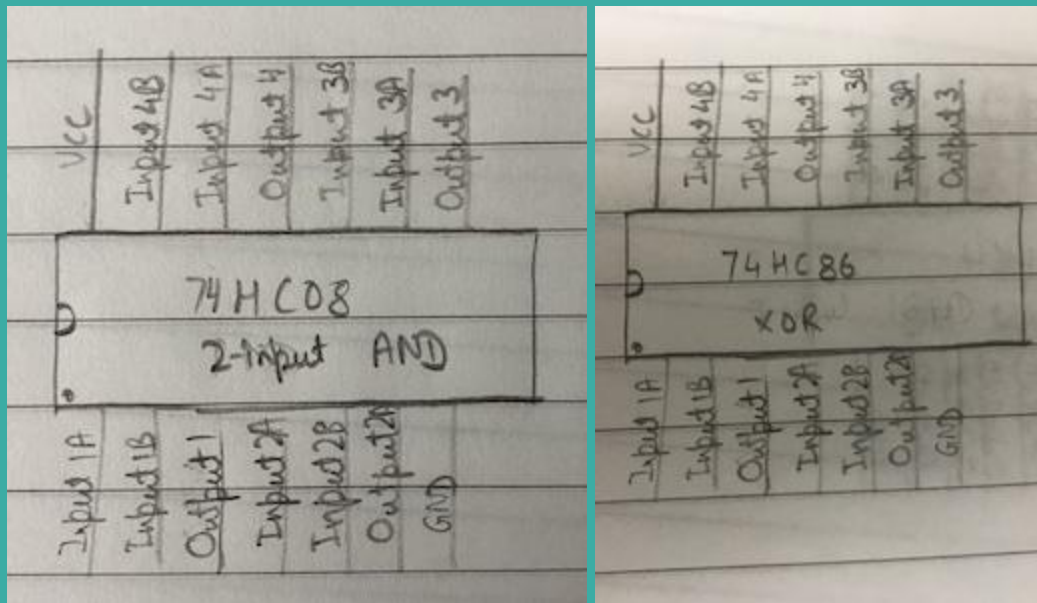

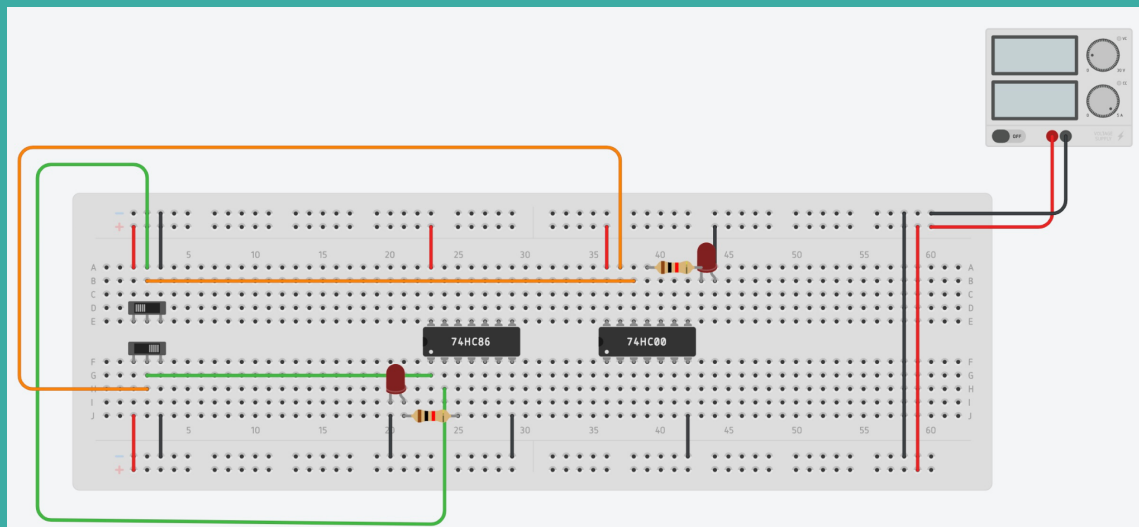Circuit Diagram: (Screenshot of Circuitverse/TinkerCAD workspace)



Truth Table:

A	B	$A \oplus B$ (Sum)	$A * B$ (Carry)
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Observations/Results: This circuit adds two binary, one-bit numbers.

Application: To add two one-bit binary numbers.

Part C: Binary full subtractor using gates

Aim: To verify that the DIFFERENCE and BORROW outputs are given by the following logic expressions:


DIFFERENCE = $A \oplus B \oplus \text{Bin}$ and

BORROW (Bout) = $A' \cdot B + (A \oplus B)' \cdot \text{Bin}$.


Components/ICs Used: Breadboard, wires, LEDs, resistors, NAND gate, OR gate, XOR gate, AND gate, slide switches, power supply.

Link of TINKERCAD Workspace (if applicable): [PartC](#)

Pin Diagram of the IC (If Applicable):

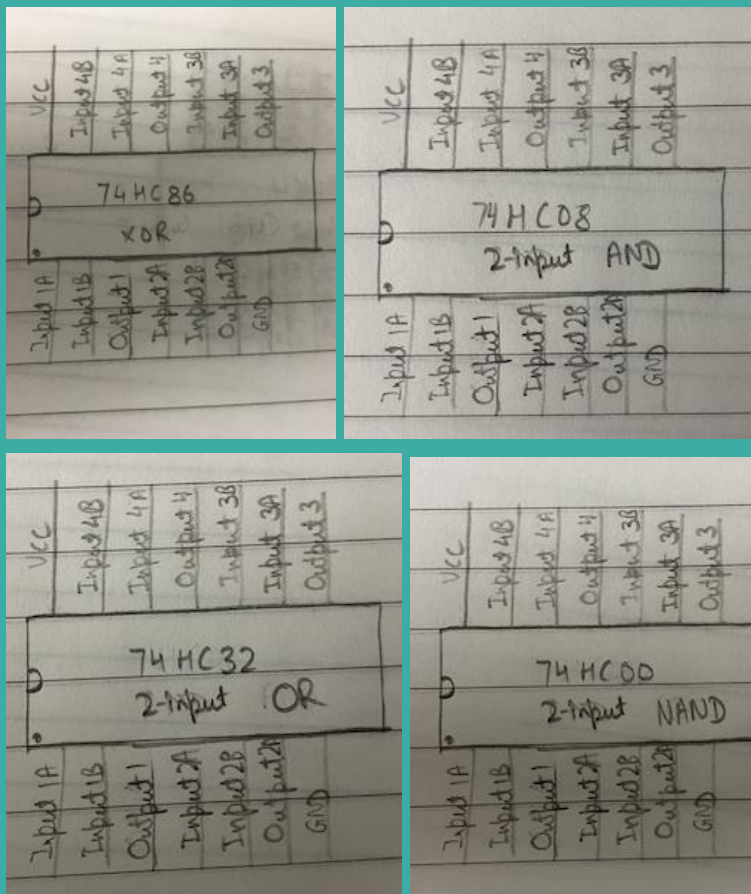

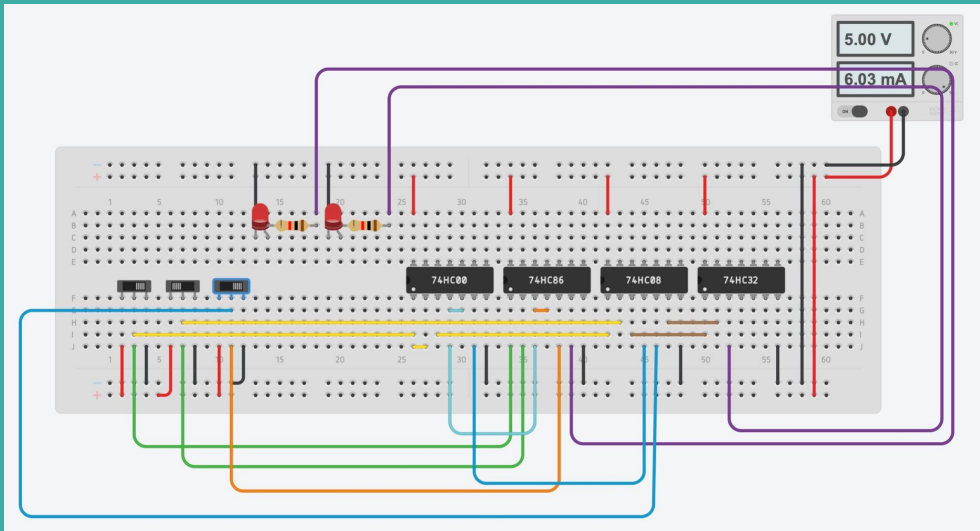Circuit Diagram: (Screenshot of Circuitverse/TinkerCAD workspace)



Truth Table:

A	B	Bin	Difference	Bout
0	0	0	0	0
0	0	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	0
1	1	1	0	0
1	1	1	1	1

Observations/Results: The logic expressions are verified

Application: To subtract to binary number with Borrow input and give difference and borrow

Problem Statement

Statement Solution:


Warning = Glass removed \oplus Weight removed

Alarm = Glass removed $*$ Weight removed


Components/ICs Used: Breadboard, wires, LEDs, resistors, slide switches, power supply, AND, XOR gate.

Link of TINKERCAD Workspace (if applicable): [ProblemSolution](#)

Pin Diagram of the IC (If Applicable):

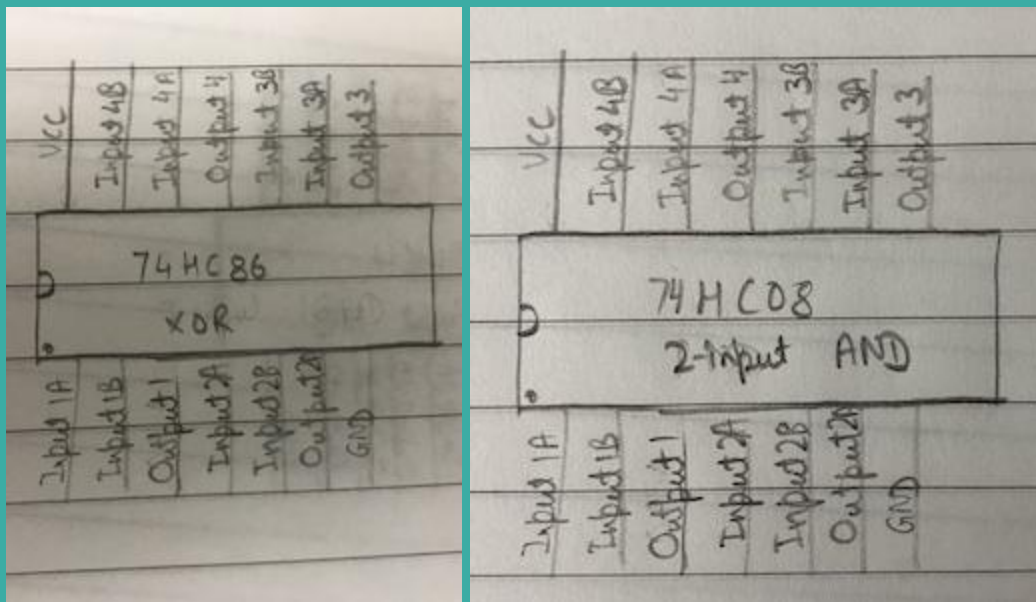

Circuit Implementation:

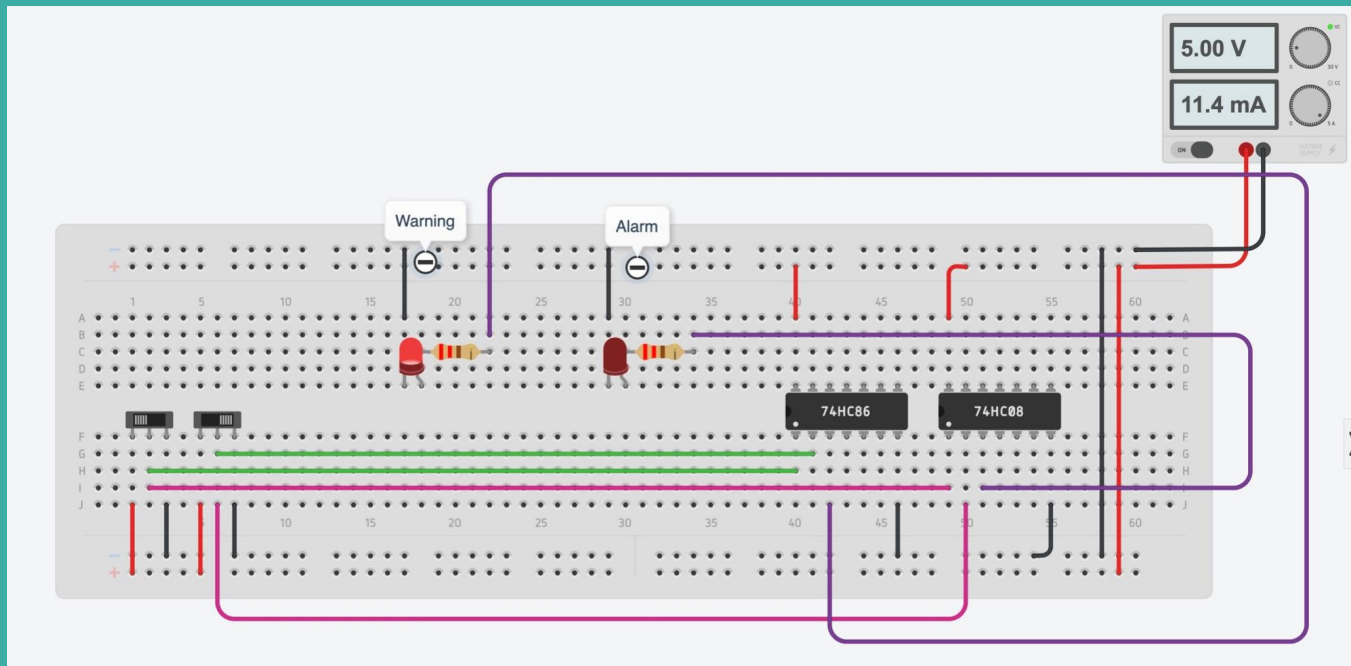

Truth Table:

Glass Removed	Weight Removed	Warning	Alarm
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1