



INDRAPRASTHA INSTITUTE *of*  
INFORMATION TECHNOLOGY  
DELHI

Department  
of  
Electronics & Communication Engineering

ECE111|Digital Circuits  
Section: B

**Dr S.S. Jamuar**

Lab\_4:

Shivoy Arora  
2021420  
7 Feb 2022

# ALU




Aim: To create a 1-bit ALU

Components/ICs Used: XOR gate, 2x1 MUX, 8x1 MUX, inputs and outputs


Link of CIRCUITVERSE Workspace:

<https://circuitverse.org/users/116502/projects/lab04-b54f429f-fbbe-45f9-8913-67fde4a4afba>

Pin Diagram of the IC:

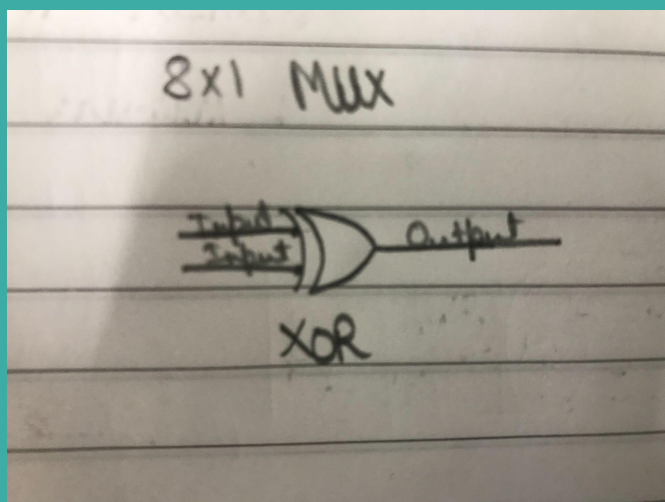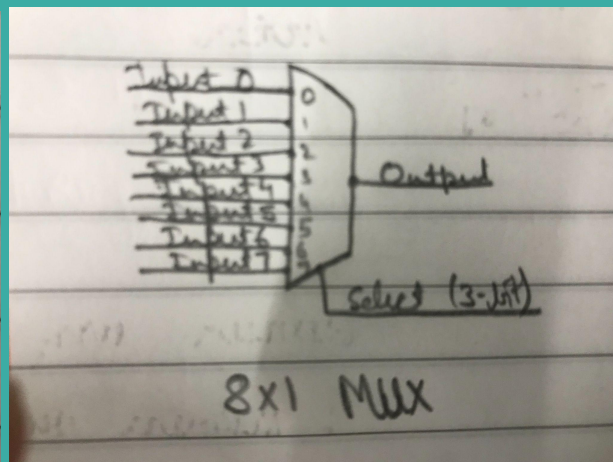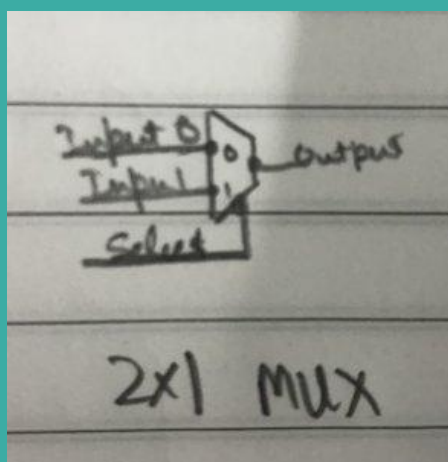

Circuit Diagram:

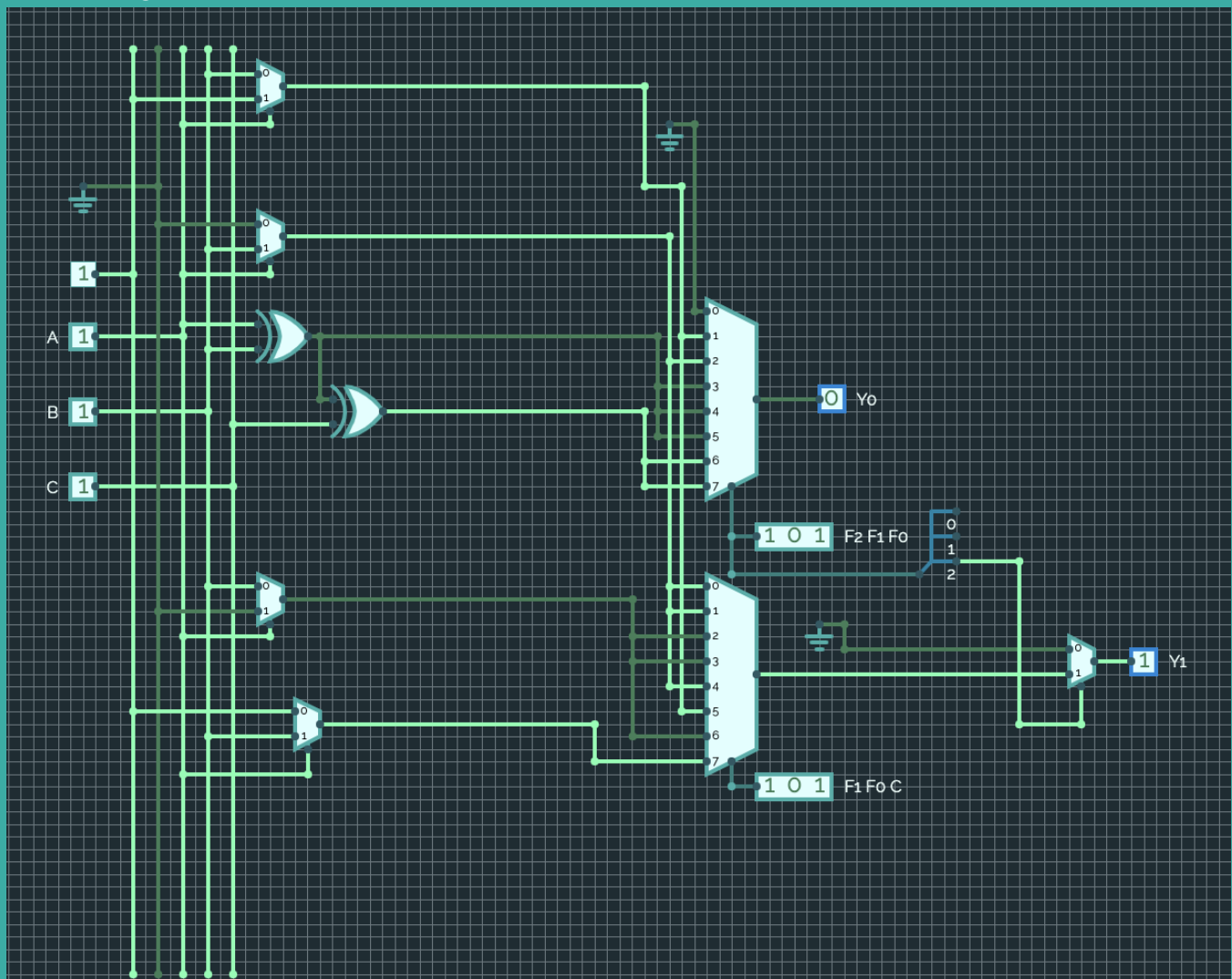

Truth Table:

2x1 MUX

Select	Output
0	I0
1	I1

### 8x1 MUX

F2	F1	F0	Output
0	0	0	I0
0	0	1	I1
0	1	0	I2
0	1	1	I3
1	0	0	I4
1	0	1	I5
1	1	0	I6
1	1	1	I7

Observations/Results: AND, OR and NOT gates can be made using 2x1 MUX

Application: A Multiplexer (MUX ) is used whenever you have multiple inputs to a circuit or a device and you have to select only one output from the given inputs.

## Problem

Solution:

Main Alarm =  $\text{input\_J} * \text{input\_K}$



Minor Alarm =  $\text{input\_L} + (\text{input\_J} \oplus \text{input\_K})$

Components/ICs Used: XOR gate, 2x1 MUX, inputs and outputs


Link of CIRCUITVERSE Workspace:

<https://circuitverse.org/users/116502/projects/lab04-b54f429f-fbbe-45f9-8913-67fde4a4afba>

Pin Diagram of the IC:

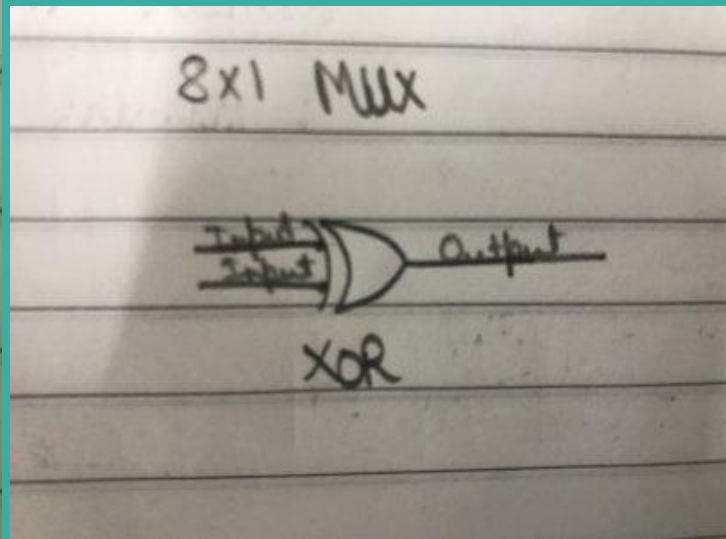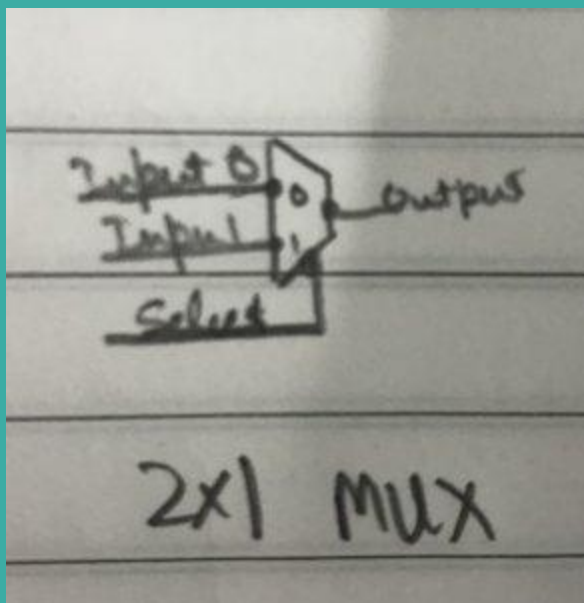

Circuit Diagram:

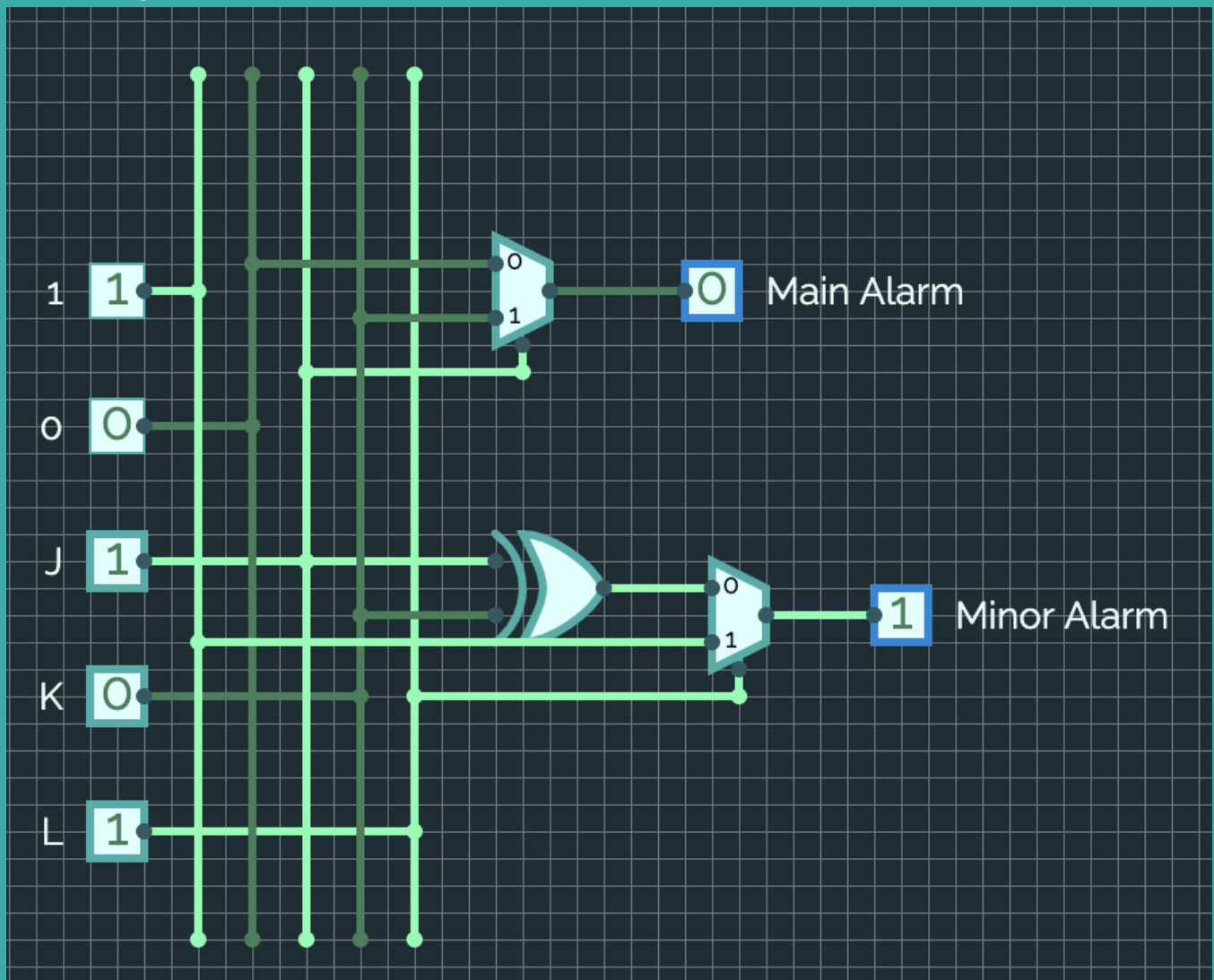

Truth Table:

J	K	L	Main Alarm	Minor Alarm
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	1	0
1	0	0	1	0
1	0	1	1	0
1	1	0	0	1
1	1	1	1	1